
2.8 INTERFACING 4X4 KEYPAD WITH LPC1768

2.8.1 INTERFACING DIAGRAM

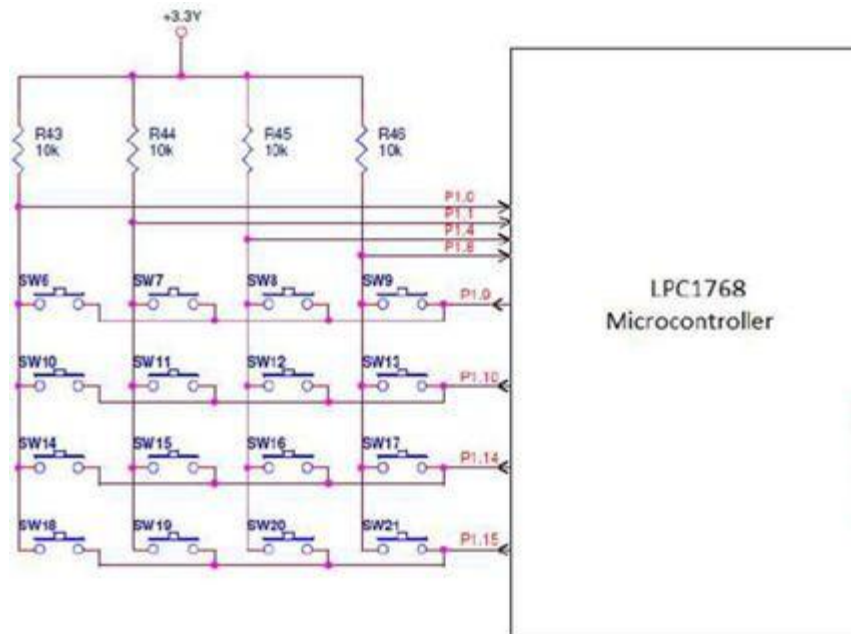


Fig.: 4x4 Keypad interfacing with LPC1768

The image shows a 4x4 keypad matrix connected to the LPC1768 microcontroller. The 4x4 keypad consists of 16 keys arranged in a matrix format of 4 rows and 4 columns.

The rows and columns are connected to GPIO pins of the microcontroller.

Working Principle of 4x4 Keypad

The working principle of the 4x4 keypad involves **scanning the rows and detecting the columns**.

1. **Rows (P1.6 to P1.9):** The rows are connected to **GPIO pins** (P1.6 to P1.9). These rows are initially **configured as output**.
 2. **Columns (P1.10 to P1.15):** The columns are connected to **GPIO pins** (P1.10 to P1.15). These columns are initially **configured as input with pull-up resistors**.
 3. **Pull-up Resistors (10kΩ):** The pull-up resistors ensure that the column pins stay **HIGH (logic 1)** when no key is pressed.
 4. **Key Press Detection:**
 - The microcontroller **sets one row LOW at a time** (by making it output LOW).
 - Then it reads the **input column pins**. If any column pin is LOW, it indicates that a key in that row is pressed.
 - This process is repeated for all four rows to identify the pressed key.
-

Example:

Suppose SW6 is pressed (Row 1, Column 1):

- The microcontroller drives **Row 1 LOW** and keeps all other rows HIGH.
- It scans the column inputs. If **Column 1** reads **LOW**, it confirms that **SW6** is pressed.

This is repeated for all keys by scanning rows one by one.

Resistor Value Calculation:

The resistors (R43, R44, R45, R46) are **pull-up resistors**, which help to keep the GPIO pins at a **logic HIGH** when no key is pressed.

1. **Pull-up Voltage (Vcc):** +3.3V
2. **Input current for GPIO Pin:** Typically, in microamperes (~0.1mA)
3. **Desired Logic HIGH Voltage:** Close to +3.3V
4. **Resistor Value (R) :** Assuming I = 0.33 mA

$$R = \frac{V_{cc}}{I} = \frac{3.3}{0.33 \times 10^{-3}} \approx 10 \text{ K}\Omega$$

Advantages of Using Pull-up Resistors:

Ensures the input pins remain HIGH when no key is pressed.

Prevents floating input which can cause unpredictable behavior.

Consumes very low current when idle.

2.8.2 EXAMPLE CODE

Write a C program for the LPC17xx microcontroller that reads the status of a 4x4 key matrix. When any switch is pressed, display the hex value of key pressed on LEDs.

```
include <LPC17xx.h>
void SetRowToZero(unsigned char);
unsigned char ReadColumnNumber(void);
void KeyPadInitialize(void); unsigned
char GetKeyPressed(void); void
delay(int count);
char keyCodes[4][4]
=
{
    {0x1,0x2,0x3,0x4},
    {0x5,0x6,0x7,0x8},
    {0x9,0xA,0xB,0xC},
    {0xD,0xE,0xF,0x0}
};
int main(void)
```

```
{    unsigned char key;

    LPC_GPIO1->FIODIR = 0x07F80000;

    KeyPadInitialize();

    while(1) //forever loop
    {
        key = GetKeyPressed();
delay(20);    // Short delay

        if (key != 0xFF) // Valid key press
LPC_GPIO1->FIOPIN = (key << 19);        else
        LPC_GPIO1->FIOCLR = 0x07F80000;
    }
} void
KeyPadInitialize(void)
{
    //Make Rows output    LPC_GPIO1->FIODIR |= (1 << 9) | (1 <<
10) | (1 << 14) | (1 << 15);

    //Make Columns as input
    LPC_GPIO1->FIODIR &= ~( (1<<0) | (1<<1) | (1<<4) | (1<<8) );
} void SetRowToZero(unsigned char
rowNumber)
{
    LPC_GPIO1->FIOSET |= (1 << 9) | (1 << 10) | (1 << 14) | (1 << 15);
    switch(rowNumber)
    {
        case 0: LPC_GPIO1->FIOCLR |= (1 << 9);
                break;
        case 1: LPC_GPIO1->FIOCLR |= (1 << 10);
                break;
        case 2: LPC_GPIO1->FIOCLR |= (1 << 14);
                break;
        case 3: LPC_GPIO1->FIOCLR |= (1 << 15);
                break;
    }
}
unsigned char ReadColumnNumber(void)
{    unsigned long int temp = LPC_GPIO1->FIOPIN;
```

```

        if((temp & (1 << 0)) == 0)
return 0;
        else if((temp & (1 << 1)) == 0)
            return 1;
        else if((temp & (1 << 4)) == 0)
            return 2;
        else if((temp & (1 << 8)) == 0)
            return 3;
else
return 4;
}  unsigned char
GetKeyPressed(void)
{    unsigned char rowNumber, colNumber;

    while(1)
    {
        for(rowNumber = 0; rowNumber < 4; rowNumber++)
        {
            SetRowToZero(rowNumber);
            colNumber = ReadColumnNumber();

            if(colNumber < 4)                return
keyCodes[rowNumber][colNumber];
        }
    }
}  void delay(int
count)
{    unsigned int i,j;

    for(i=0; i<count; i++)
for(j=0; j<1275; j++);
}

```

Further exploration:

Display the key pressed on LCD
